

TEAM 1


1. Joshua Rayadu
(PES2UG25AM120)
2. Kaarthik Viswanath
(PES2UG25C\$243)
3. KB Tanag Sai
(PES2UG25AM122)
4. MANOJ KOTTE
(PES2UG25AM132)
5. MAHANTHESH C K
(PES2UG25CS287)

ELECTRICAL ENGINEERING

POWERING TODAY, ENERGIZING TOMORROW

$$V = IR$$
$$P = VI = I^2 R = \frac{V^2}{R}$$
$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$
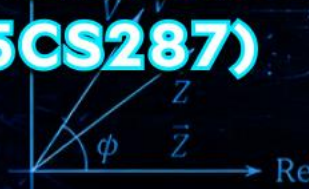
$$X_L = \omega L, \quad X_C = \frac{1}{\omega C}$$
$$\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t}$$
$$\nabla \times \vec{H} = \vec{J} + \frac{\partial \vec{D}}{\partial t}$$




QUESTION:

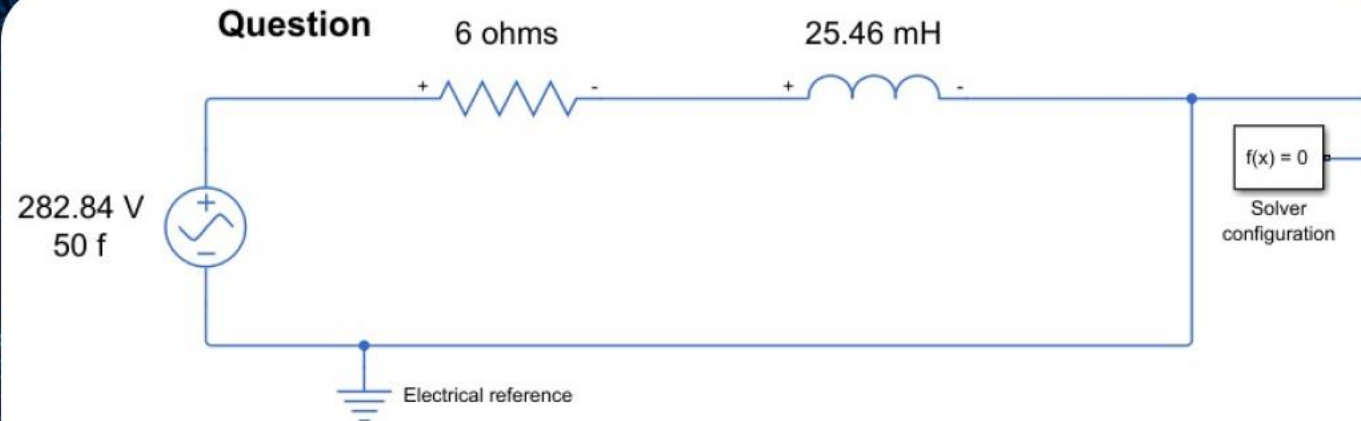1. A resistor of 6Ω and an ideal inductor 25.46mH are connected in series across 200V , 50 Hz supply. Determine

- Supply current
- Active, Reactive and Apparent powers supplied by the source

Obtain the waveforms of source voltage, supply current, voltage across the resistor and voltage across the inductor using SIMULINK and also validate the values of Active, Reactive and Apparent powers supplied by the source using SIMULINK.




Given:

- Resistance,
 $R = 6\Omega$
- Inductance,
 $L = 25.46\text{ mH}$
- Supply
Voltage,
 $V = 200\text{V}$
- Frequency,
 $f = 50\text{ Hz}$

MANUAL SOLVING:

1.

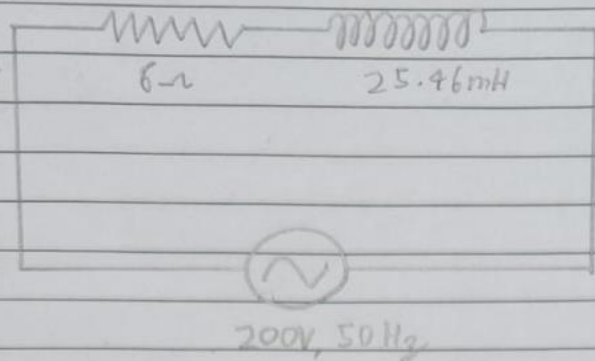

Given:

$$R = 6\Omega$$

$$L = 25.46\text{ mH}$$

$$V = 200\text{ V}$$

$$f = 50\text{ Hz}$$

$$X_L = \omega L = L(2\pi f) = (25.46 \times 10^{-3})(2\pi \times 50) \\ \approx 8\Omega$$

$$|Z| = \sqrt{R^2 + X_L^2} = 10\Omega$$


$$\text{i) } I = \frac{V}{|Z|} = \frac{200}{10} = 20\text{ A}$$

$$\text{ii) } P = I^2 R = (20)^2 (6) = \cancel{2} \times 2400\text{ W} = 2.4\text{ kW}$$


$$Q = I^2 X_L = (20)^2 (8) = 3200\text{ VAR} = 3.2\text{ kVAR}$$

$$S = \sqrt{P^2 + Q^2} = \sqrt{(2.4)^2 + (3.2)^2} = 4\text{ kVA}$$


Supply Current (RMS)

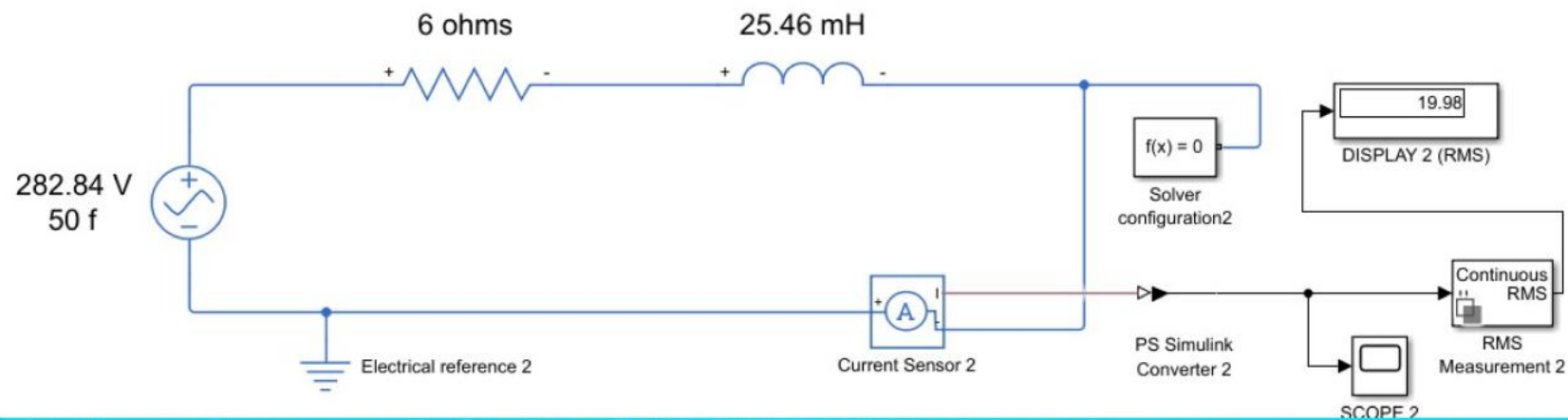


Source Voltage (RMS)

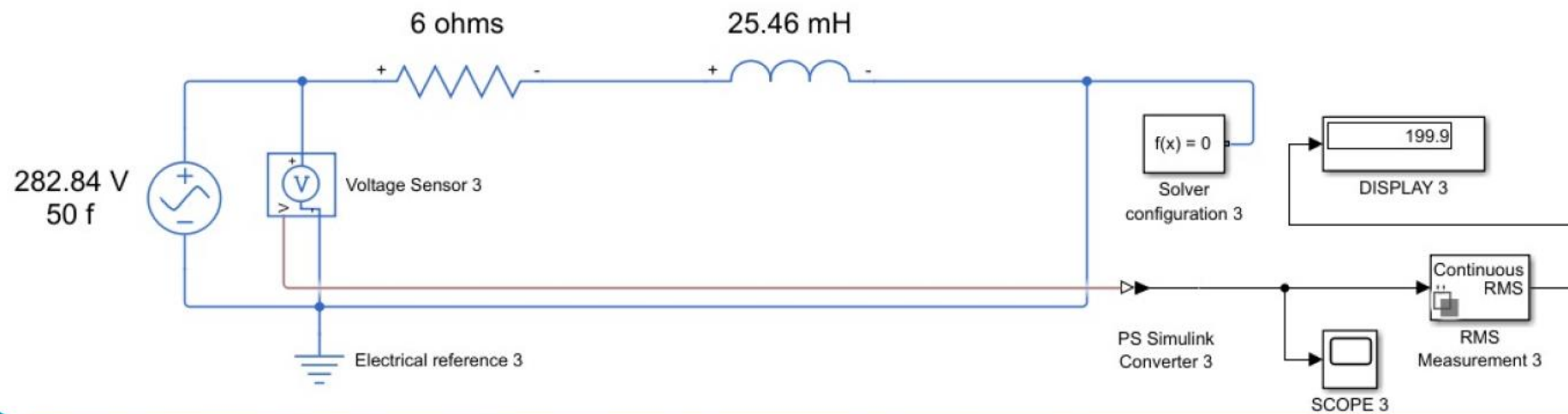


Voltage across resistor (RMS)

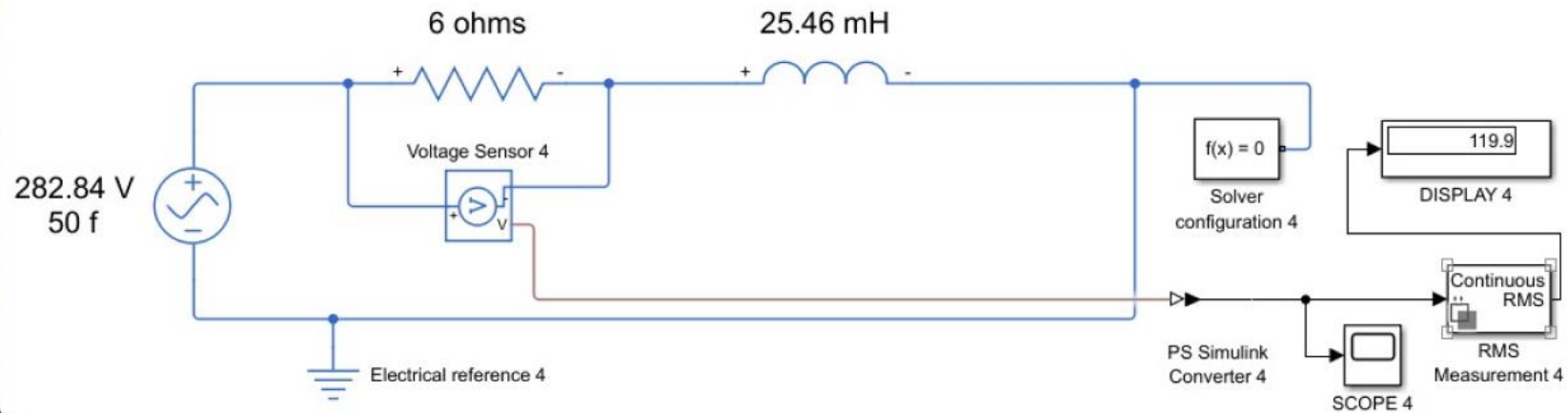


Voltage across inductor (RMS)

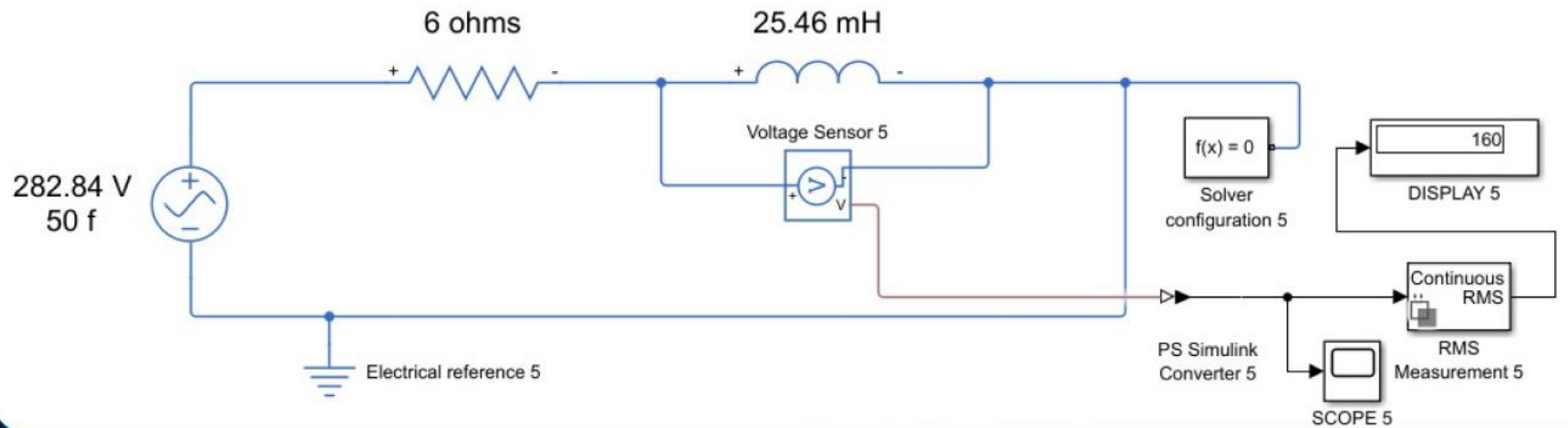


Active Power

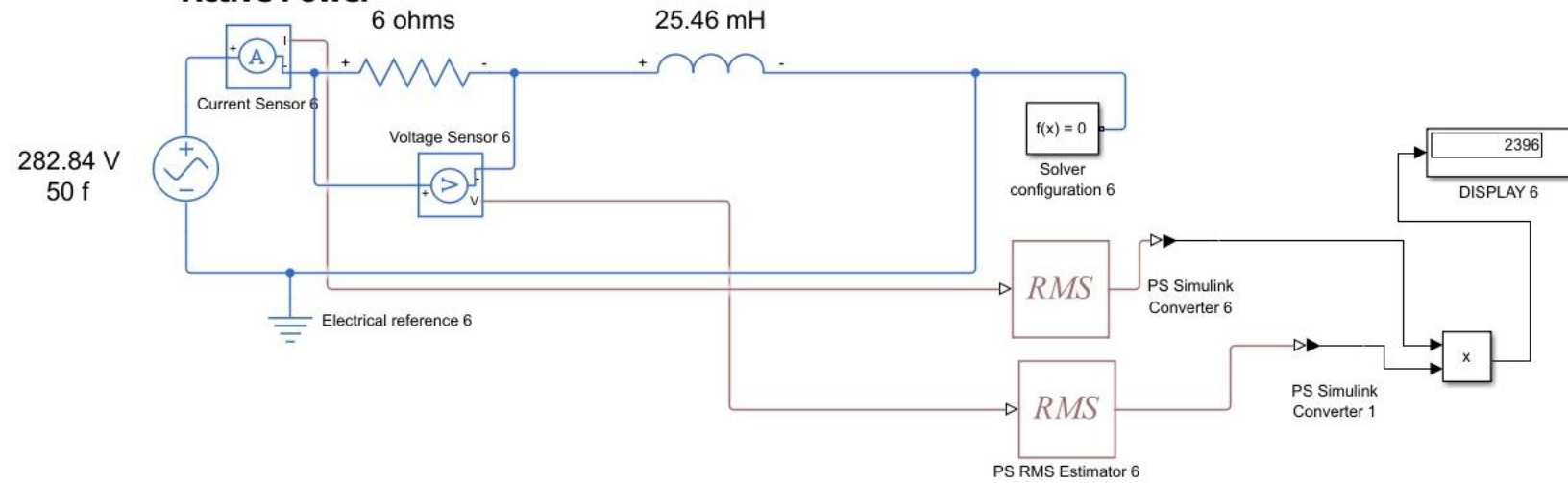


Reactive Power

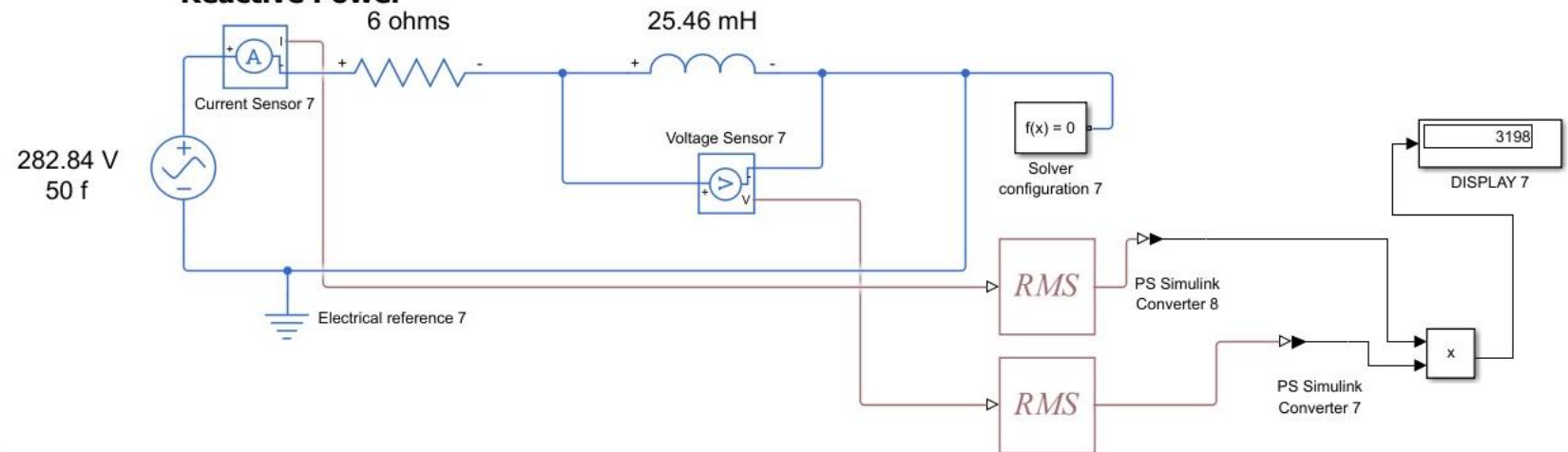


Apparent Power

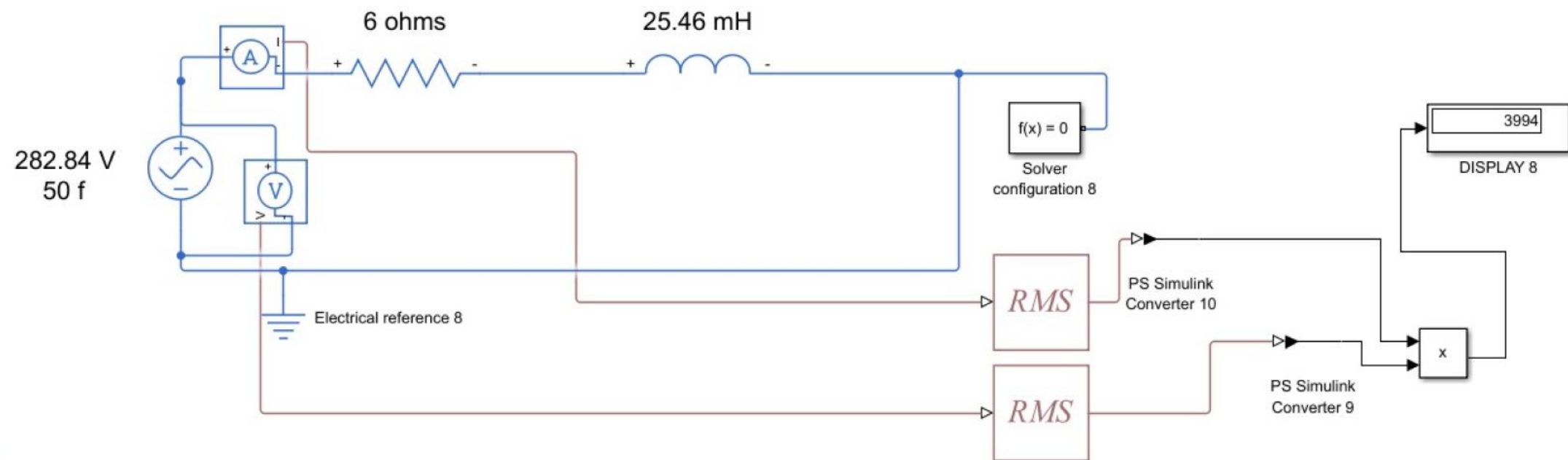


Supply Current (RMS)

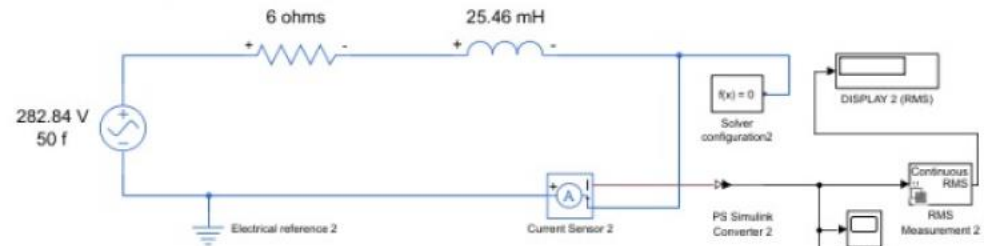



Source Voltage (RMS)

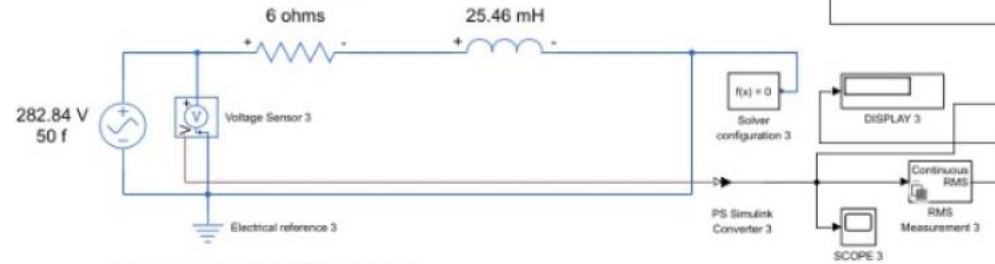


Voltage across resistor (RMS)

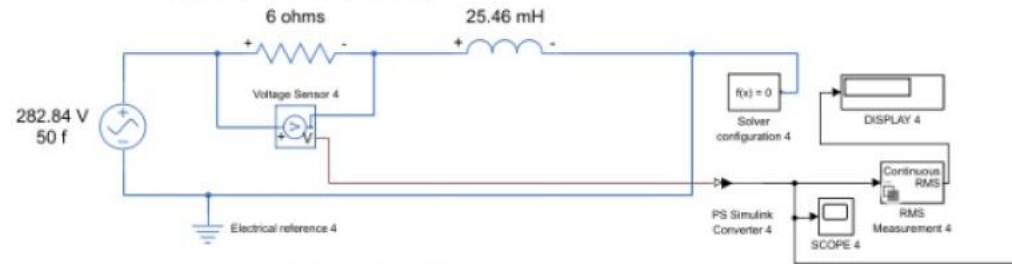

Voltage across inductor (RMS)

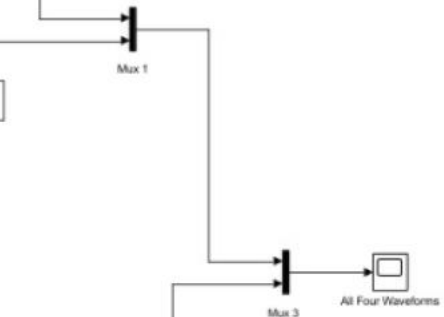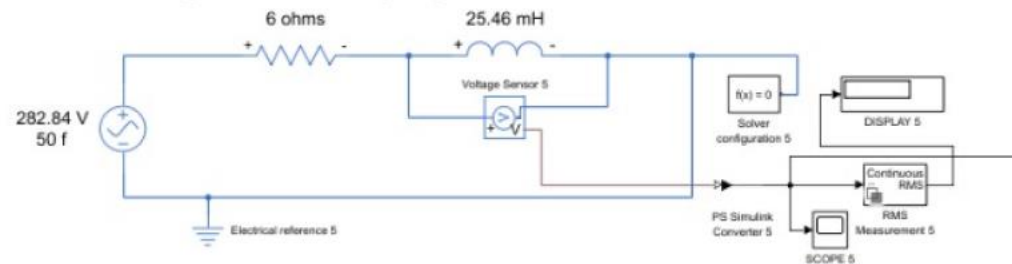

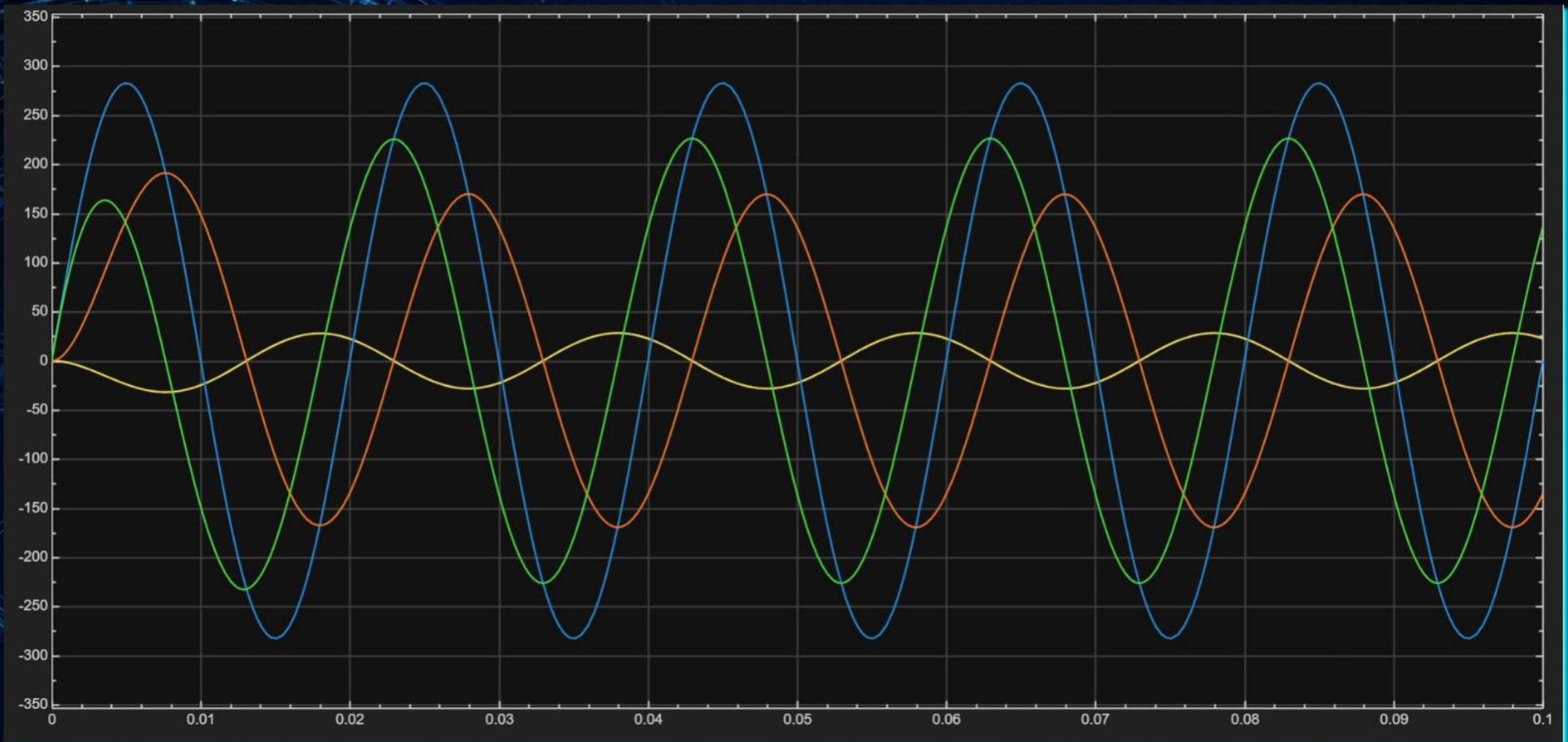

Comparison of Manually Calculated Values vs Simulink Results

Parameter	Manually Calculated Value	Simulink Result (RMS)	Absolute Difference	Percentage Error (%)
Supply Current (I) (RMS)	20.00 A	19.98 A	0.02 A	0.10 %
Source Voltage (V _s) (RMS)	200.00 V	199.90 V	0.10 V	0.05 %
Voltage across Resistor (V _R) (RMS)	120.00 V	119.90 V	0.10 V	0.08 %
Voltage across Inductor (V _L) (RMS)	160.00 V	160.00 V	0.00 V	0.00 %
Active Power (P)	2.40 kW	2.396 kW	0.004 kW	0.17 %
Reactive Power (Q)	3.20 kVAR	3.198 kVAR	0.002 kVAR	0.06 %
Apparent Power (S)	4.00 kVA	3.994 kVA	0.006 kVA	0.15 %
Power Factor (cos ϕ)	0.60 (Lagging)	0.60 (Lagging)	–	–
Impedance (Z)	10.00 Ω	10.00 Ω	0.00 Ω	0.00 %
Inductive Reactance (X _L)	8.00 Ω	8.00 Ω	0.00 Ω	0.00 %